

Codefest 6

CMAN — Sneak Paths in a Resistive Crossbar

(a) In order for current to reach ground on col 0 it must only pass through the top 1 k Ω resistor (ideally) and hence by Ohm's law:

$$I_{\text{col0}} = 1\text{V} / 1\text{k}\Omega = \mathbf{1\text{ mA}} \text{ output.}$$

(b) Since row 0 is kept at 1V, the current can also travel via the sneak path which jumps to col 1 via the 2 k Ω resistor, then on to row 1 via the 1 k Ω resistor, and then to ground via the 2 k Ω resistor. Hence:

$$I_{\text{sneak}} = V / (R_2 + R_3 + R_4) = 1\text{V} / 5\text{ k}\Omega = \mathbf{0.2\text{ mA}}$$

$$V_{\text{row1}} = I_{\text{sneak}} \times R_3 = 2/5\text{ mV} = \mathbf{0.4\text{ mV}}$$

As for V_{col1} , start with V_{row0} at 1V and dropping through the 2 k Ω resistor gives:

$$V_{\text{col1}} = (1 - 2/5)\text{ V} = 3/5\text{ V} = \mathbf{0.6\text{ V}}$$

(c) $I_{\text{col0}} = I_{\text{ideal}} + I_{\text{sneak}} = (1 + 0.2)\text{ mA} = \mathbf{1.2\text{ mA}}$

(d) Ideally, the current in each column should be only a function of the values of the resistors that lie in that column. This is what makes this model work as a matrix-vector multiply algorithm. With the sneak current this is no longer strictly true.